

ECE 478 Laboratory Work #4

- 1) Design an even parity detector state machine for a sequence consisting of N bits. Implement your state machine in VHDL.
- 2) Draw the state machine of "010" non-overlapping detector. Implement your circuit in VHDL.
- 3) Arbiters are used to manage access to shared resources. An example is depicted in Figure 1, which shows three peripherals (P1 to P3) that use a common bus to access common resources.

Obviously, only one of them can use the bus at a time; for example, if P1 wants to use the bus, it issues a request ($r_1 = 1'$) to the arbiter, which grants ($g_1 = 1'$) access only if the bus is idle at that moment.

If multiple requests are received by the arbiter, access is granted based on pre-established priorities. Assuming that the priorities are $P1 > P2 > P3$, draw a state transition diagram for a machine capable of implementing this arbiter. The machine's input and output are the vectors $r = r_1 r_2 r_3$ and $g = g_1 g_2 g_3$, respectively (besides clock and reset, of course).

Implement the state machine of the arbiter in VHDL.

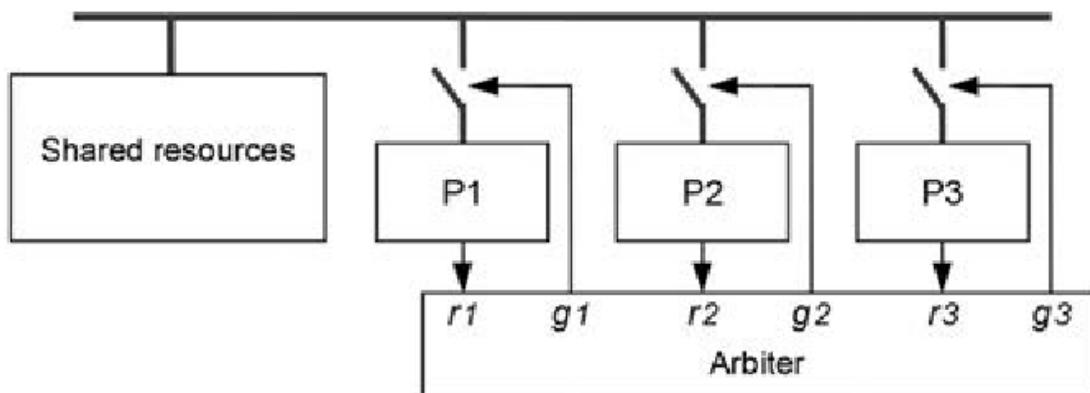


Fig-1